



Εθνικό Μετσόβιο Πολυτεχνείο
Σχολή Ηλεκτρολόγων Μηχανικών και Μηχανικών
Υπολογιστών
Εξάμηνο: 8^ο Ακ.
Έτος: 2024- 2025

«Ψηφιακά Συστήματα VLSI»

Χαράλαμπος Παπαδόπουλος (ΑΜ: 03120199)
Νικόλαος Παπακωνσταντόπουλος (ΑΜ: 03120069)

Ομάδα: 45

BCD Parallel Adder

Ζητούμενο αυτής της άσκησης ήταν η υλοποίηση ενός BCD Parallel Adder 4 ψηφίων, ο οποίος παίρνει 2 Binary Coded Decimal αριθμούς των 4 ψηφίων (δηλαδή από 0 έως 9999) και τους αθροίζει κάνοντας διόρθωση στην έξοδο μέσω του c_{out} .

Η άσκηση ακολούθησε μία bottom up λογική, δηλαδή σε κάθε ερώτημα μας ζητούταν να σχεδιάσουμε ένα κύκλωμα το οποίο θα χρησιμοποιούταν ως δομική μονάδα σε ένα πιο περίπλοκο κύκλωμα μέσω structural αρχιτεκτονικής.

Παρατίθενται οι κώδικες κάθε υποερωτήματος, μαζί με τα αντίστοιχα RTL, testbench και critical paths.

i) Half Adder


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity half_adder is
    Port (
        A, B          : in  std_logic;
        sum, cout      : out std_logic
    );
end half_adder;

architecture dataflow of half_adder is

begin
    sum <= A XOR B;
    cout <= A AND B;

end dataflow;
```

 

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity half_adder_tb is
end half_adder_tb;

architecture test of half_adder_tb is
    component half_adder
        Port (
            A, B          : in std_logic;
            sum, cout     : out std_logic
        );
    end component;

    signal A, B          : std_logic;
    signal sum, cout     : std_logic;



begin
    uut: half_adder
        port map (
            A => A,
            B => B,
            sum => sum,
            cout => cout
        );

    process
    begin
        A <= '0'; B <= '0'; wait for 10 ns;
        A <= '0'; B <= '1'; wait for 10 ns;
        A <= '1'; B <= '0'; wait for 10 ns;
        A <= '1'; B <= '1'; wait for 10 ns;

        wait;
    end process;

end test;

```

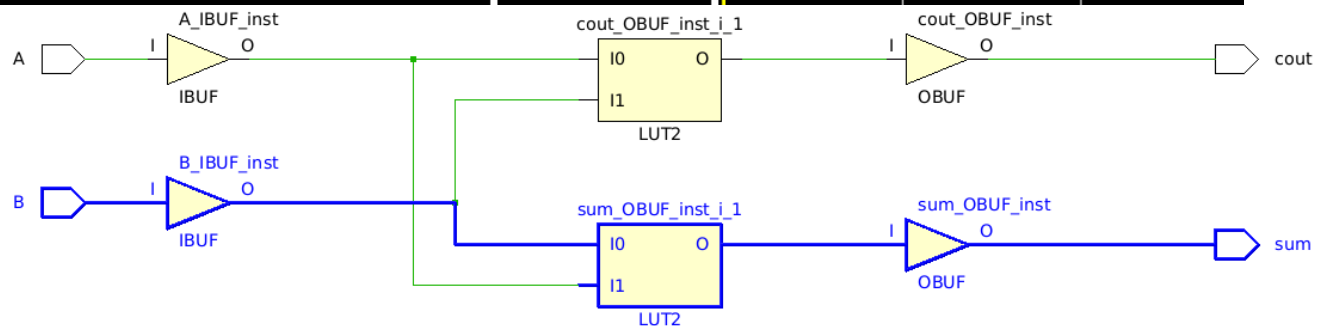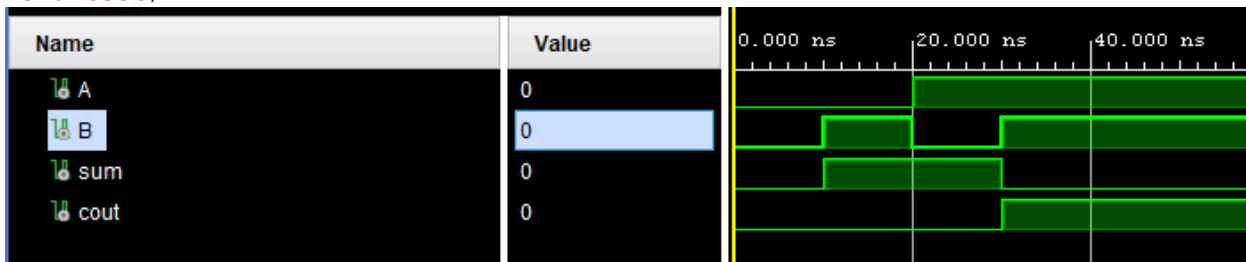

Unconstrained Paths - NONE - NONE - Setup													
Path	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception
Path 1	∞	3	4	2	B	sum	5.377	3.778	1.599	∞	input port clock		

Critical Path: B → sum 5.377 ns

ii) Full adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity full_adder is
    Port (
        A, B, cin : in std_logic;
        sum, cout : out std_logic
    );
end full_adder;

architecture structural of full_adder is

    component half_adder
        Port (
            A, B : in std_logic;
            sum, cout : out std_logic
        );
    end component;

    signal sum1, c1, c2 : std_logic;

begin


    HA1: half_adder
        port map (
            A => A,
            B => B,
            sum => sum1,
            cout => c1
        );

    HA2: half_adder
        port map (
            A => sum1,
            B => cin,
            sum => sum,
            cout => c2
        );

    cout <= c1 OR c2;

end structural;

```

 

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity full_adder_tb is
end full_adder_tb;
architecture testbench of full_adder_tb is

    component full_adder
        Port (
            A, B, cin : in  std_logic;
            sum, cout  : out std_logic
        );
    end component;

    signal A, B, cin : std_logic := '0';
    signal sum, cout : std_logic;


begin


    uut: full_adder
        port map (
            A    => A,
            B    => B,
            cin  => cin,
            sum  => sum,
            cout => cout
        );

    process
    begin
        A <= '0'; B <= '0'; Cin <= '0'; wait for 10 ns;
        A <= '0'; B <= '0'; Cin <= '1'; wait for 10 ns;
        A <= '0'; B <= '1'; Cin <= '0'; wait for 10 ns;
        A <= '0'; B <= '1'; Cin <= '1'; wait for 10 ns;
        A <= '1'; B <= '0'; Cin <= '0'; wait for 10 ns;
        A <= '1'; B <= '0'; Cin <= '1'; wait for 10 ns;
        A <= '1'; B <= '1'; Cin <= '0'; wait for 10 ns;
        A <= '1'; B <= '1'; Cin <= '1'; wait for 10 ns;

        wait;
    end process;
end testbench;

```

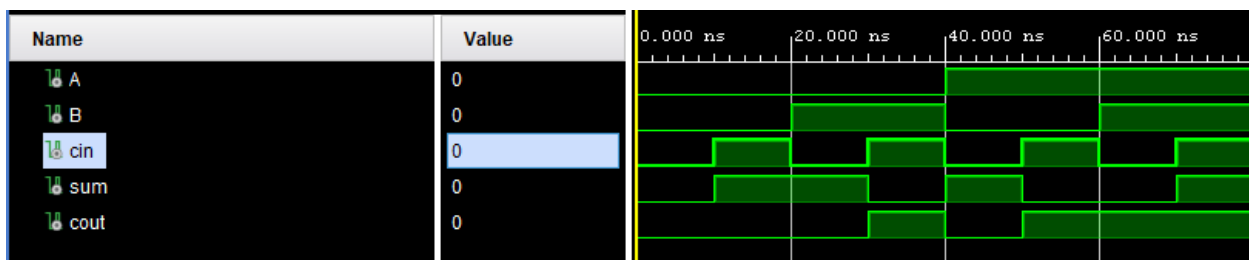

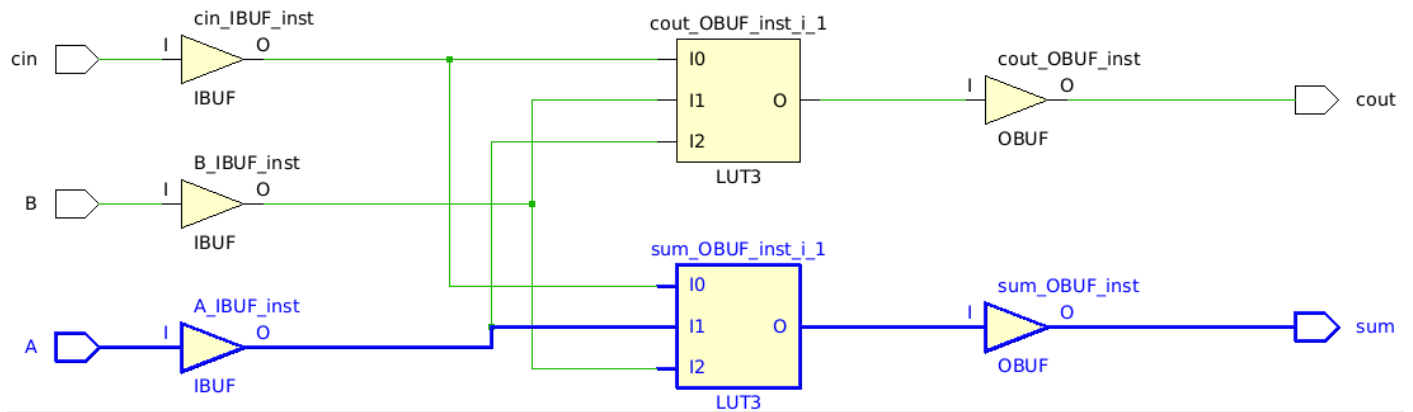

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exc
Path 1	∞	3	4	2	A	sum	5.377	3.778	1.599	∞	input port clock		

Critical Path: A → sum 5.377 ns (ίσο με πριν, από είσοδο ως sum)

iii) Parallel Adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity parallel_adder is
    Port (
        A, B          : in  std_logic_vector(4-1 downto 0);
        cin           : in  std_logic;
        sum           : out std_logic_vector(4-1 downto 0);
        cout          : out std_logic
    );
end parallel_adder;

architecture structural of parallel_adder is

    component full_adder is
        Port (
            A, B, cin : in  std_logic;
            sum, cout : out std_logic
        );
    end component;

    signal c1, c2, c3 : std_logic;
begin
    FA1: full_adder
        port map(
            A  => A(0),
            B  => B(0),
            cin => cin,
            cout => c1,
            sum  => sum(0)
        );

    FA2: full_adder
        port map(
            A  => A(1),
            B  => B(1),
            cin => c1,
            cout => c2,
            sum  => sum(1)
        );


```

```

FA3: full_adder
    port map(
        A    => A(2),
        B    => B(2),
        cin  => c2,
        cout => c3,
        sum  => sum(2)
    );

FA4: full_adder
    port map(
        A    => A(3),
        B    => B(3),
        cin  => c3,
        cout => cout,
        sum  => sum(3)
    );
end structural;

```

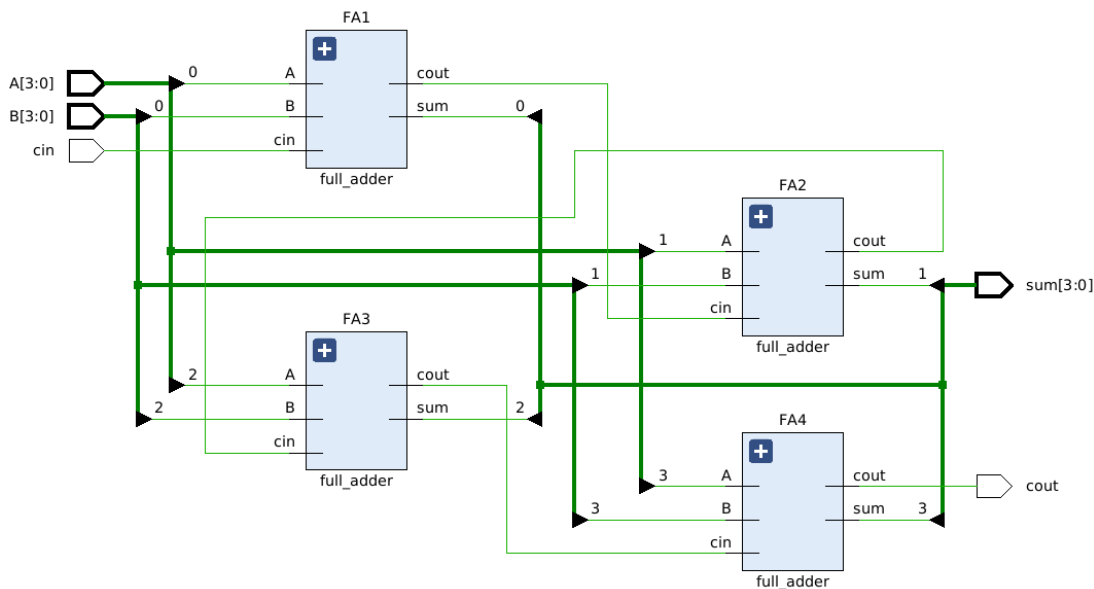

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity parallel_adder_tb is
end parallel_adder_tb;

architecture testbench of parallel_adder_tb is

    component parallel_adder
        Port (
            A, B : in  std_logic_vector(3 downto 0);
            cin  : in  std_logic;
            sum  : out std_logic_vector(3 downto 0);
            cout : out std_logic
        );
    end component;

    signal A, B : std_logic_vector(3 downto 0);
    signal cin  : std_logic;
    signal sum  : std_logic_vector(3 downto 0);
    signal cout : std_logic;

```



```

begin
    uut: parallel_adder
        port map (
            A    => A,
            B    => B,
            cin  => cin,
            sum  => sum,
            cout => cout
        );

    process
    begin
        A <= "0000"; B <= "0000"; cin <= '0'; wait for 10 ns; -- 0 + 0
        A <= "0001"; B <= "0001"; cin <= '0'; wait for 10 ns; -- 1 + 1
        A <= "0010"; B <= "0011"; cin <= '0'; wait for 10 ns; -- 2 + 3
        A <= "0110"; B <= "0010"; cin <= '1'; wait for 10 ns; -- 6 + 2 + 1
        A <= "1010"; B <= "0101"; cin <= '0'; wait for 10 ns; -- 10 + 5
        A <= "1111"; B <= "1111"; cin <= '0'; wait for 10 ns; -- 15 + 15
        A <= "1111"; B <= "1111"; cin <= '1'; wait for 10 ns; -- 15 + 15 + 1

        wait;
    end process;
end testbench;

```

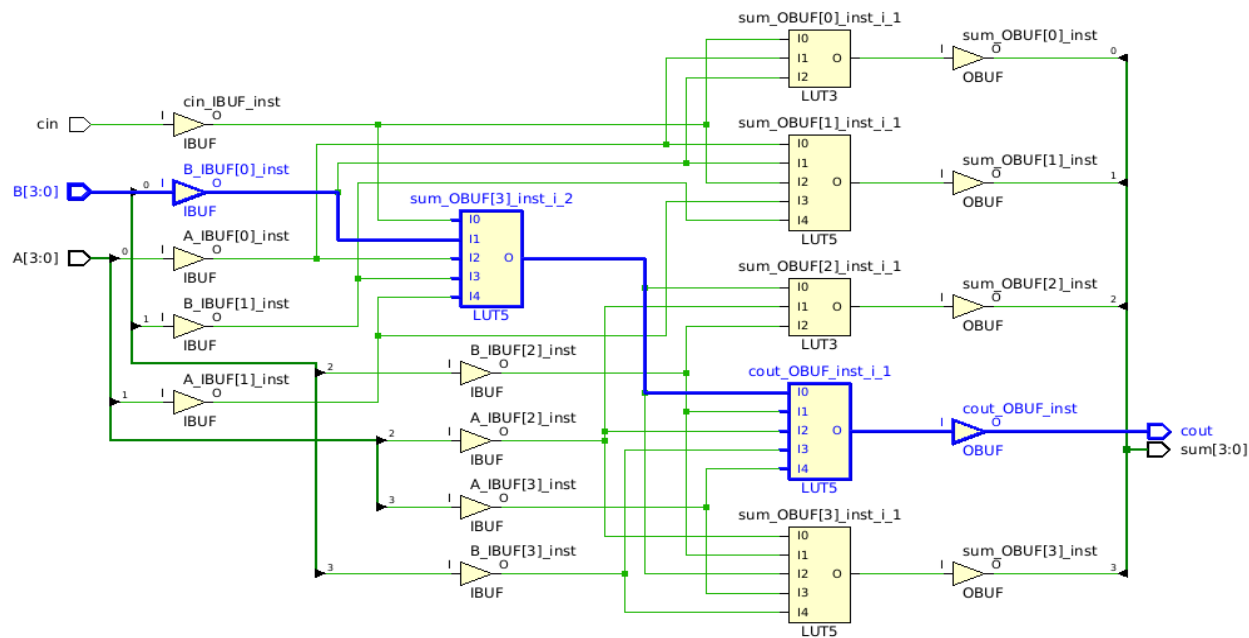 

Unconstrained Paths - NONE - NONE - Setup											
Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	4	5	3	B[0]	cout	5.970	3.904	2.066	∞	input port clock

Critical Path: $B \rightarrow c_{out}$ 5.970 ns

iv) BCD Full Adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity BCD_full_adder is
    Port (
        A, B      : in  std_logic_vector(4-1 downto 0);
        cin       : in  std_logic;
        sum       : out std_logic_vector(4-1 downto 0);
        c3, cn    : inout std_logic
    );
end BCD_full_adder;

architecture structural of BCD_full_adder is

    signal sum1, B1 : std_logic_vector(3 downto 0);
    signal cn_int   : std_logic;
    signal or_input : std_logic_vector(2 downto 0);

    component parallel_adder is
        Port (
            A, B      : in  std_logic_vector(4-1 downto 0);
            cin       : in  std_logic;
            sum       : out std_logic_vector(4-1 downto 0);
            cout      : out std_logic
        );
    end component;

begin

    PA1: parallel_adder
        port map(
            A    => A,
            B    => B,
            sum  => sum1,
            cin  => cin,
            cout => c3
        );


    B1 <= ('0' & cn_int & cn_int & '0');    -- second input of second PA

    PA2: parallel_adder
        port map(
            A    => sum1,
            B    => B1,
            sum  => sum,
            cin  => '0'
        );

    cn_int <= ( c3 OR (sum1(3) AND sum1(2)) OR (sum1(3) and sum1(1)) );
    cn <= cn_int;

end structural;

```

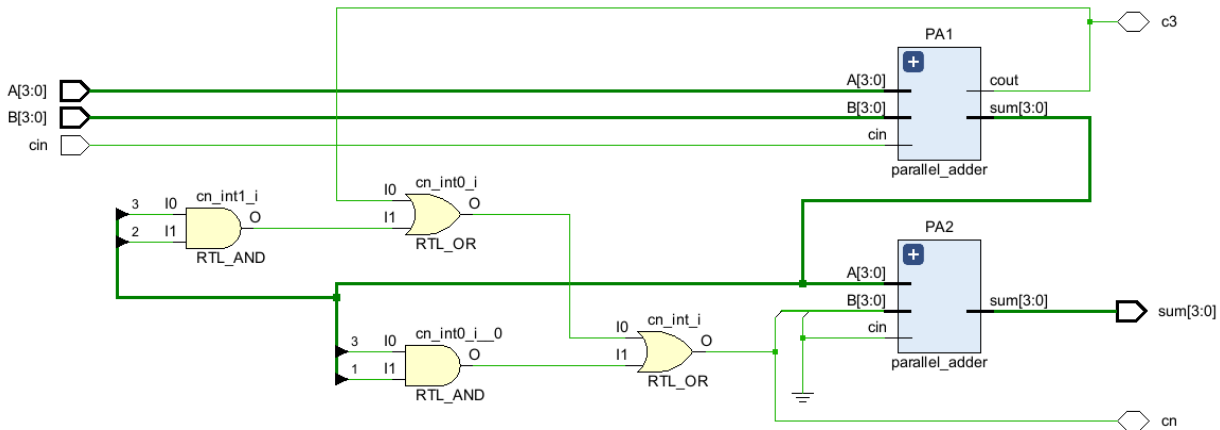

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity BCD_full_adder_tb is
end BCD_full_adder_tb;

architecture test of BCD_full_adder_tb is

    component BCD_full_adder
        Port (
            A, B : in std_logic_vector(3 downto 0);
            cin : in std_logic;
            sum : out std_logic_vector(3 downto 0);
            c3, cn: inout std_logic
        );
    end component;

    signal A, B, sum : std_logic_vector(3 downto 0);
    signal cin, c3, cn : std_logic;

begin

    uut: BCD_full_adder
        port map (
            A => A,
            B => B,
            cin => cin,
            sum => sum,
            c3 => c3,
            cn => cn
        );

    process
    begin
        A <= "0101"; -- 5
        B <= "0011"; -- 3
        cin <= '0';
        wait for 10 ns;

        A <= "0111"; -- 7
        B <= "1001"; -- 9
        cin <= '0';
        wait for 10 ns;

        A <= "1000"; -- 8
    end process
end architecture test;

```

```

    B   <= "0101";  -- 5
    cin <= '0';
    wait for 10 ns;


    A   <= "1001";  -- 9
    B   <= "1001";  -- 9
    cin <= '1';
    wait for 10 ns;

    wait;
end process;

end test;

```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns
> A[3:0]	9	5	7	8		9
> B[3:0]	9	3	9	5		9
> sum[3:0]	9	8	6	3		9
cin	1					
c3	1					
cn	1					

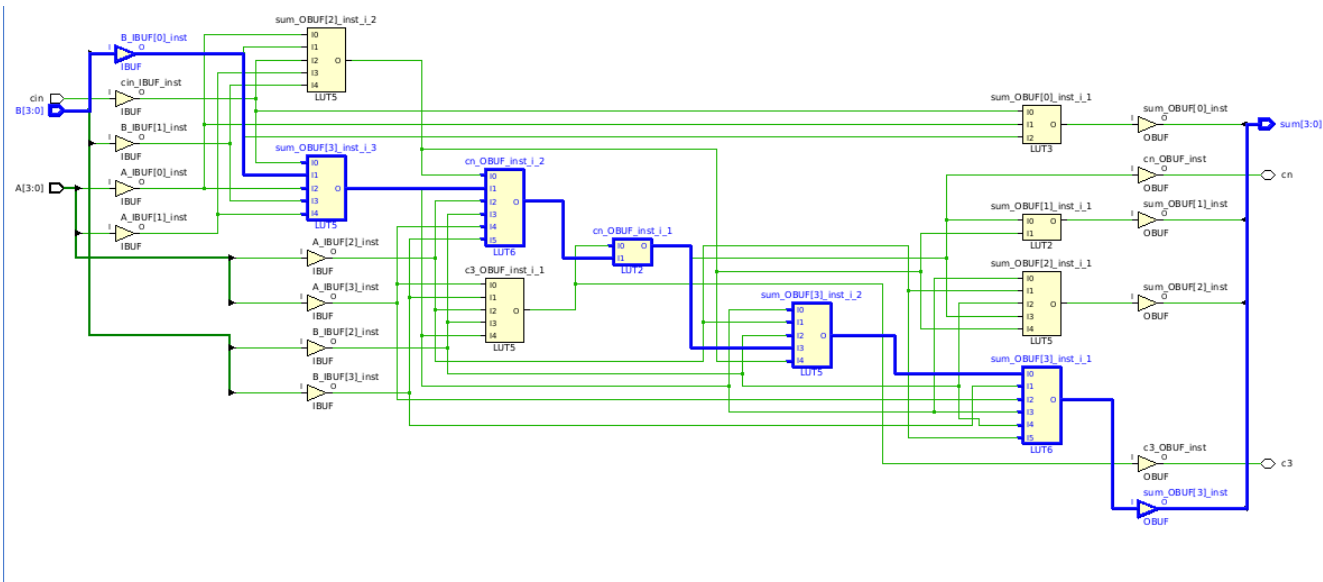

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception	Cl
Path 1	∞	7	8	5	B[0]	sum[3]	7.717	4.270	3.447	∞	input port clock			

Critical Path: B → sum 7.717 ns

v) BCD Parallel Adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity BCD_parallel_adder is
    Port (
        A0, B0      : in  std_logic_vector(4-1 downto 0);
        A1, B1      : in  std_logic_vector(4-1 downto 0);
        A2, B2      : in  std_logic_vector(4-1 downto 0);
    );
end entity BCD_parallel_adder;

```

```

    A3, B3      : in std_logic_vector(4-1 downto 0);
    cin         : in std_logic;
    S0          : out std_logic_vector(4-1 downto 0);
    S1          : out std_logic_vector(4-1 downto 0);
    S2          : out std_logic_vector(4-1 downto 0);
    S3          : out std_logic_vector(4-1 downto 0);
    cout        : inout std_logic
  );
end BCD_parallel_adder;

architecture Behavioral of BCD_parallel_adder is
  signal cout_0, cout_1, cout_2 : std_logic;

  component BCD_full_adder is
    Port (
      A, B      : in std_logic_vector(4-1 downto 0);
      cin       : in std_logic;
      sum       : out std_logic_vector(4-1 downto 0);
      c3, cn    : inout std_logic
    );
  end component;

begin

  BCD_FA1: BCD_full_adder
    port map(
      A    => A0,
      B    => B0,
      sum  => S0,
      cin  => cin,
      cn   => cout_0
    );


  BCD_FA2: BCD_full_adder
    port map(
      A    => A1,
      B    => B1,
      sum  => S1,
      cin  => cout_0,
      cn   => cout_1
    );

  BCD_FA3: BCD_full_adder
    port map(
      A    => A2,
      B    => B2,
      sum  => S2,
      cin  => cout_1,
      cn   => cout_2
    );

  BCD_FA4: BCD_full_adder
    port map(
      A    => A3,
      B    => B3,
      sum  => S3,
      cin  => cout_2,
      cn   => cout
    );

end Behavioral;

```

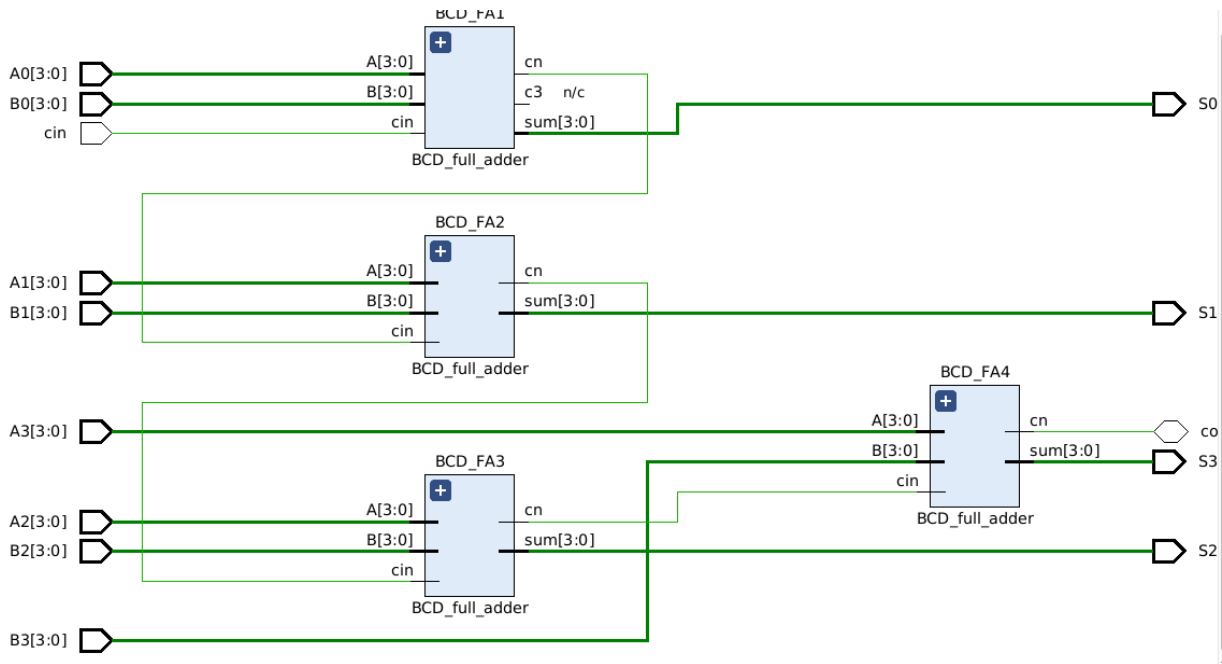

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED;

entity BCD_parallel_adder_tb is
end BCD_parallel_adder_tb;

architecture test of BCD_parallel_adder_tb is

    component BCD_parallel_adder is
        Port (
            A0, B0      : in  std_logic_vector(4-1 downto 0);
            A1, B1      : in  std_logic_vector(4-1 downto 0);
            A2, B2      : in  std_logic_vector(4-1 downto 0);
            A3, B3      : in  std_logic_vector(4-1 downto 0);
            cin         : in  std_logic;
            S0          : out std_logic_vector(4-1 downto 0);
            S1          : out std_logic_vector(4-1 downto 0);
            S2          : out std_logic_vector(4-1 downto 0);
            S3          : out std_logic_vector(4-1 downto 0);
            cout        : inout std_logic
        );
    end component;

    signal A0, B0, A1, B1, A2, B2, A3, B3, S0, S1, S2, S3 : std_logic_vector(4-1
downto 0);
    signal cin, cout : std_logic;

begin
    uut: BCD_parallel_adder
        port map (
            A0  => A0,
            B0  => B0,
            A1  => A1,
            B1  => B1,
            A2  => A2,
            B2  => B2,
            A3  => A3,
            B3  => B3,

```

```

        cin => cin,
        S0  => S0,
        S1  => S1,
        S2  => S2,
        S3  => S3,
        cout => cout
    );

process
    type test_array is array(0 to 2) of integer range 0 to 15;
    constant tests : test_array := (
        0, 5, 9
    );
begin
    for i in 0 to 2 loop
        for x in 0 to 2 loop
            for y in 0 to 2 loop

                B3 <= std_logic_vector(to_unsigned(tests(i), 4));
                B2 <= std_logic_vector(to_unsigned(tests(i), 4));
                B1 <= std_logic_vector(to_unsigned(tests(i), 4));
                B0 <= std_logic_vector(to_unsigned(tests(i), 4));

                A3 <= std_logic_vector(to_unsigned(tests(x), 4));
                A2 <= std_logic_vector(to_unsigned(tests(x), 4));
                A1 <= std_logic_vector(to_unsigned(tests(y), 4));
                A0 <= std_logic_vector(to_unsigned(tests(y), 4));



                cin <= '0';
                wait for 10 ns;

                cin <= '1';
                wait for 10 ns;

            end loop;
        end loop;
    end loop;
    wait;
end process;

end test;

```

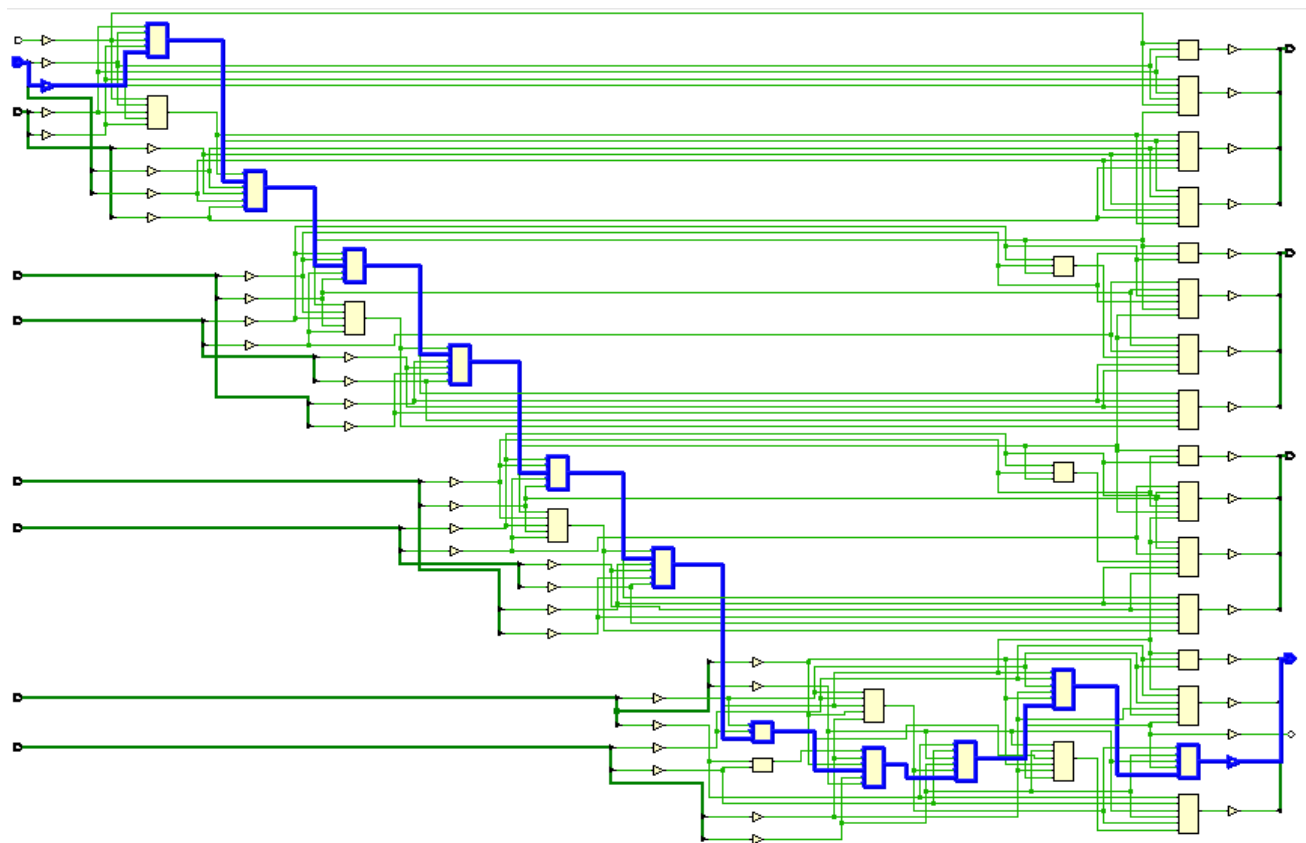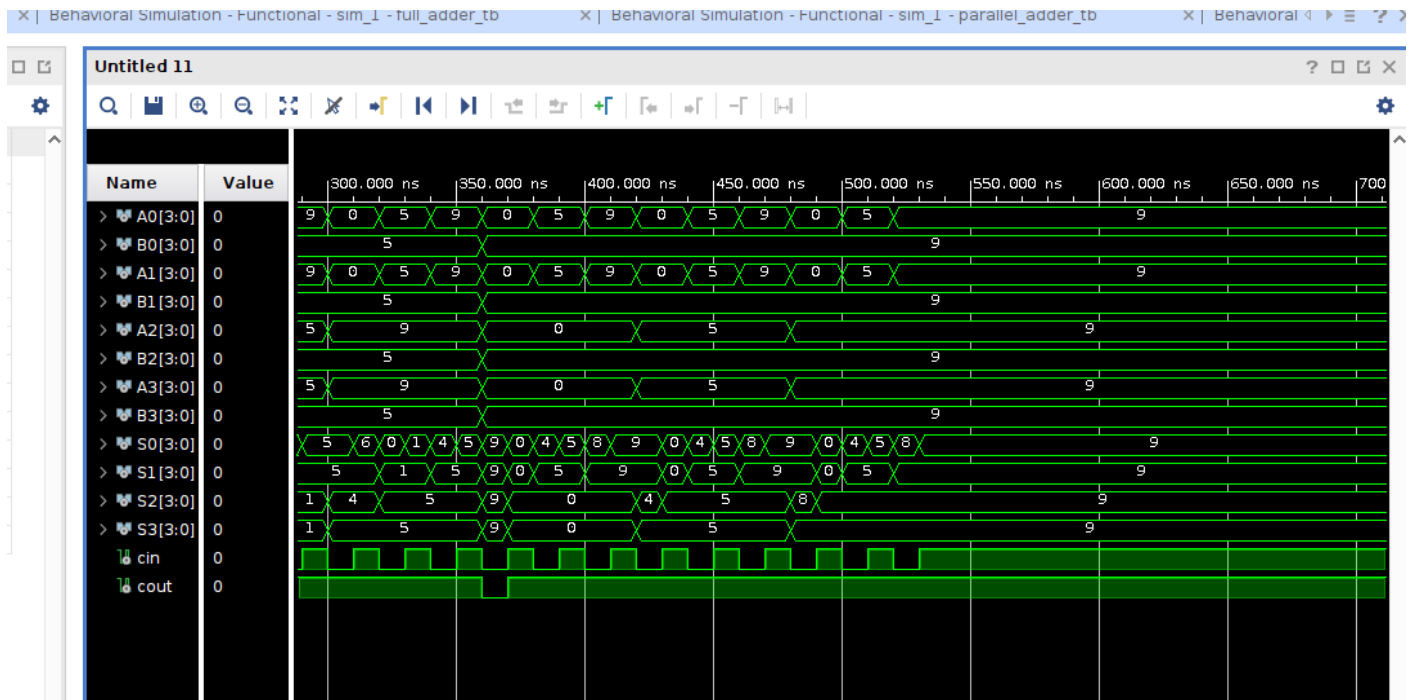

Unconstrained Paths - NONE - NONE - Setup

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source
Path 1	∞	13	14	7	B0[1]	S3[2]	11.262	4.992	6.270	∞	input

Critical Path: B0 → S3 11.262ns